


# Fundamentals of Computer Systems

## A Multicycle MIPS Processor

Harris and Harris  
Chapter 7.4


Illustrations Copyright © 2007 Elsevier

# State Elements

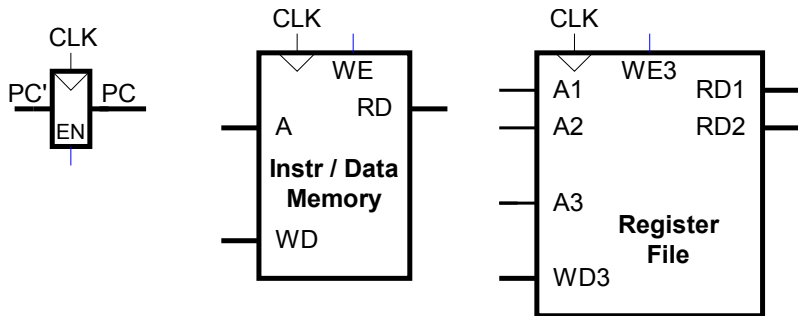


# Multicycle Datapath

Fetch instruction from memory

 


# Multicycle Datapath

Read source operands from register file

 


# Multicycle Datapath

Sign-extend the immediate

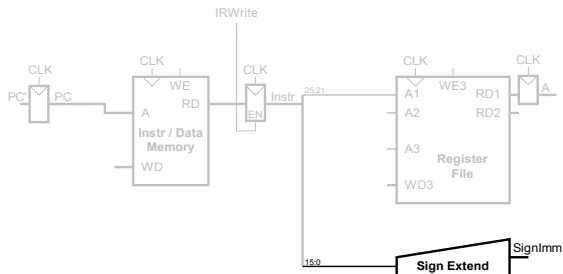


# Multicycle Datapath

Add base address to offset

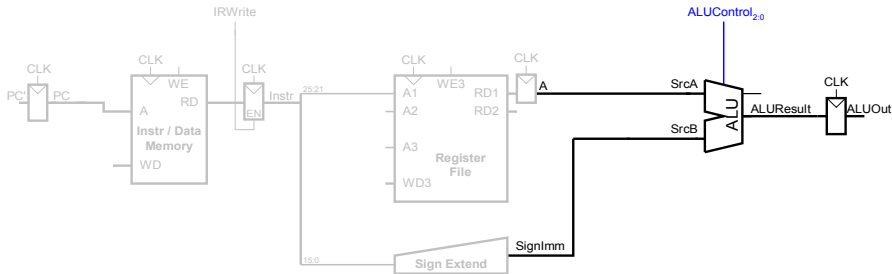


# Multicycle Datapath

Load data from memory

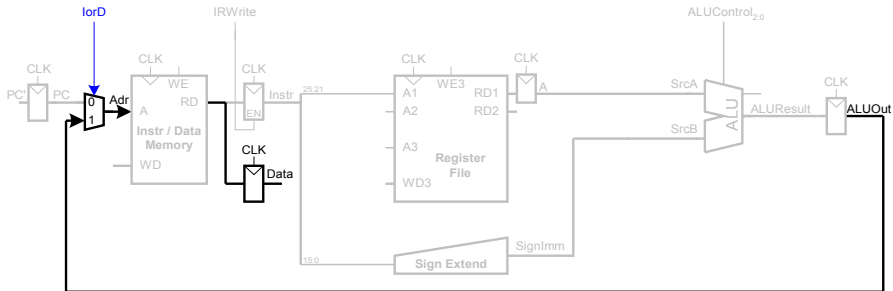

# Multicycle Datapath


Write data back to register file

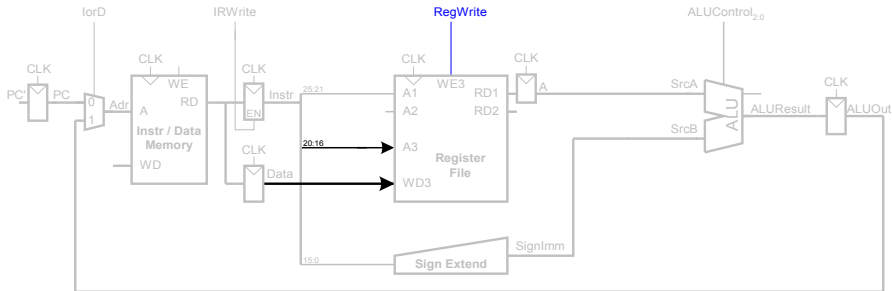




# Multicycle Datapath

Add 4 to PC

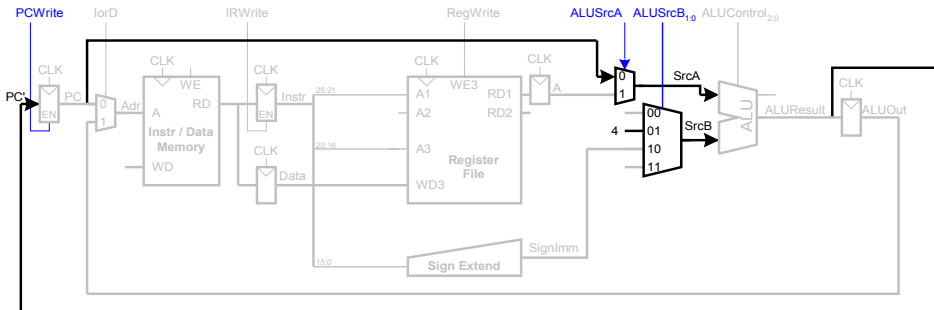


# Multicycle Datapath

For sw: Write register data to memory

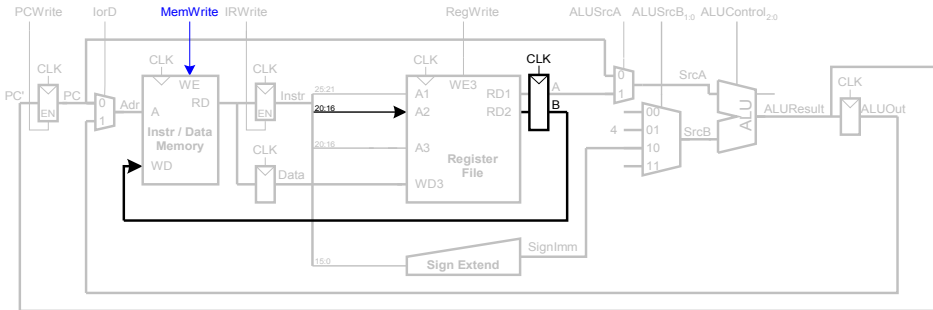

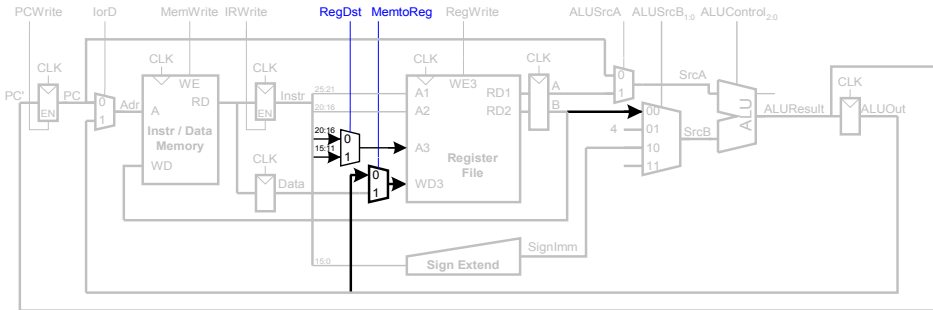
# Multicycle Datapath

For R-type instructions: Write ALU result to registers




# Multicycle Datapath

For bne: Add immediate to PC

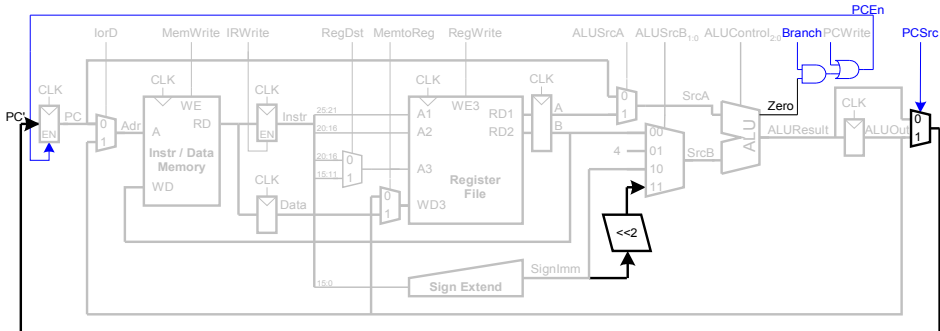


# Multicycle Datapath

## Add Controller

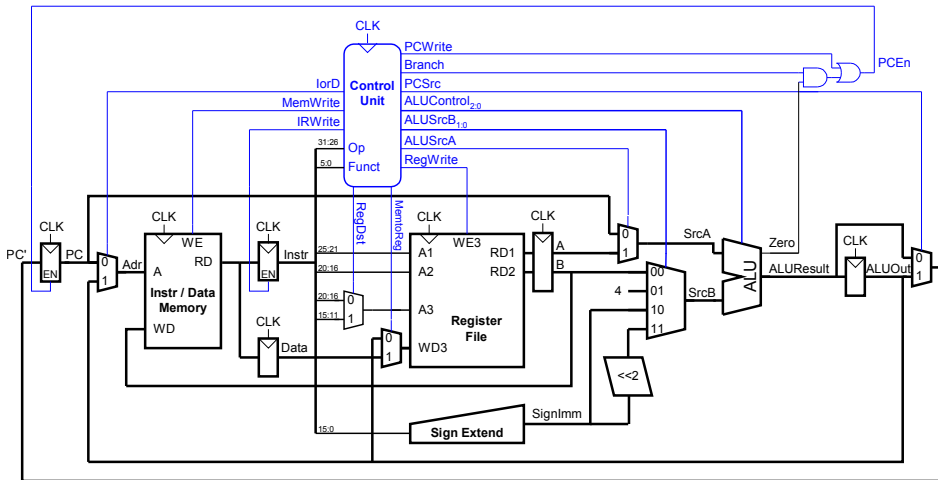


# Controller Internals

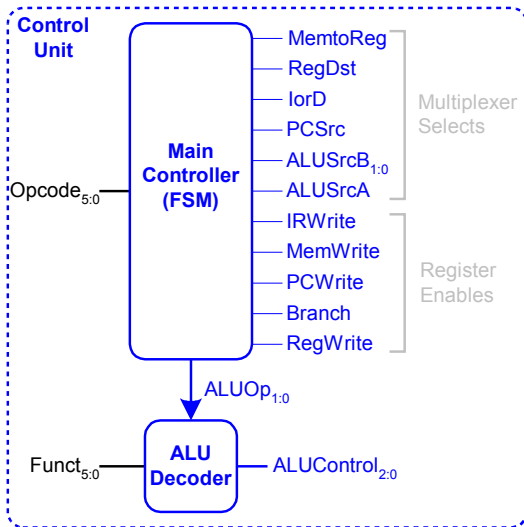



# Controller Behavior



Fetch

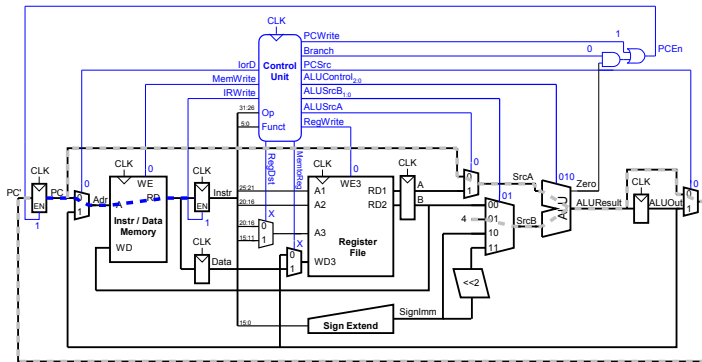


## Controller Behavior

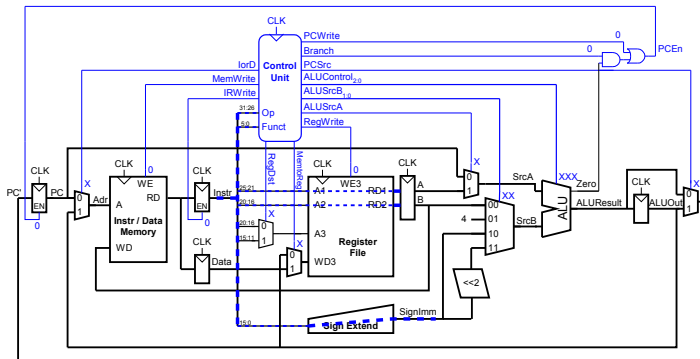 





# Controller Behavior

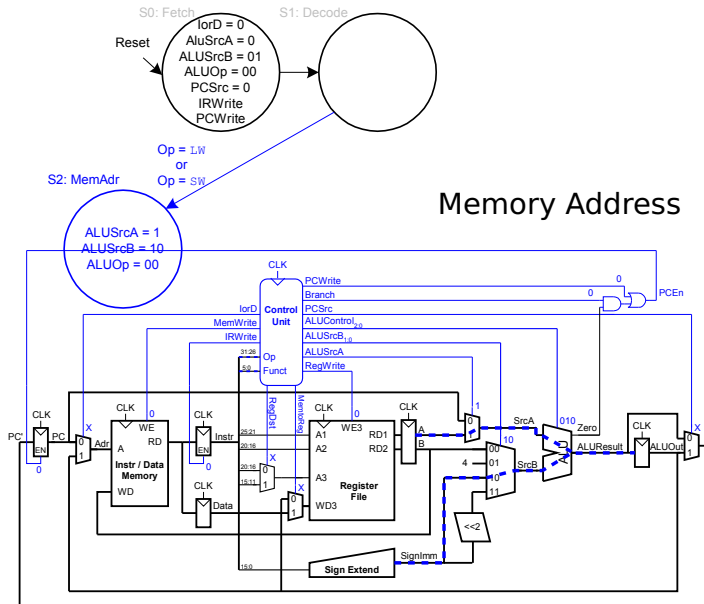


# Controller Behavior

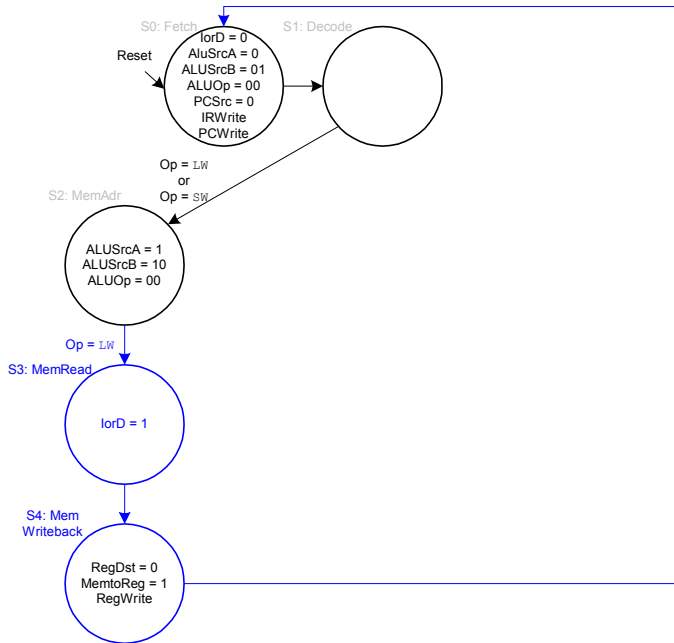


# Controller Behavior

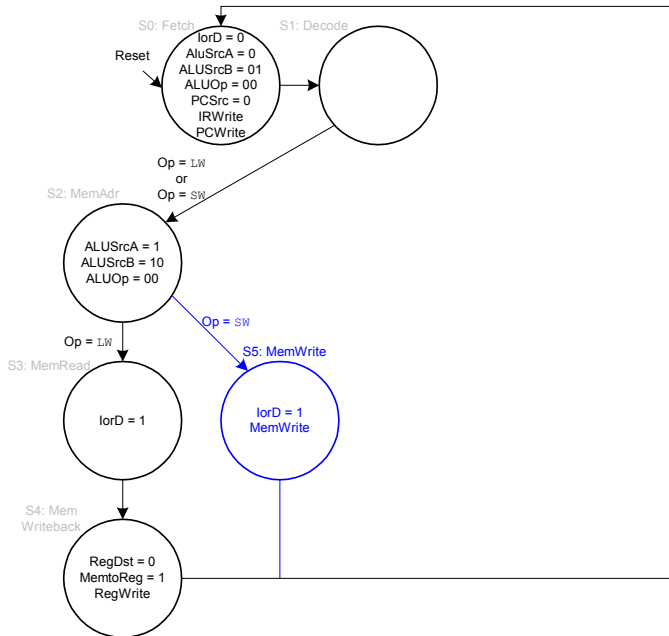


# Controller Behavior

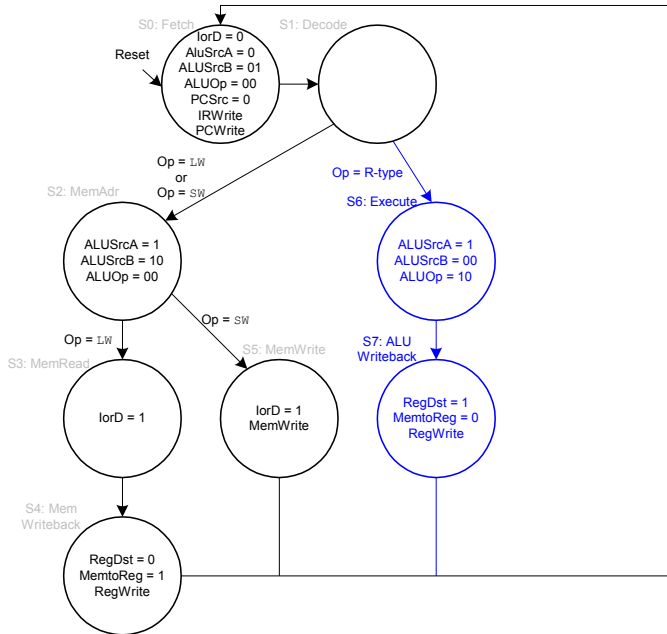

# Controller Behavior

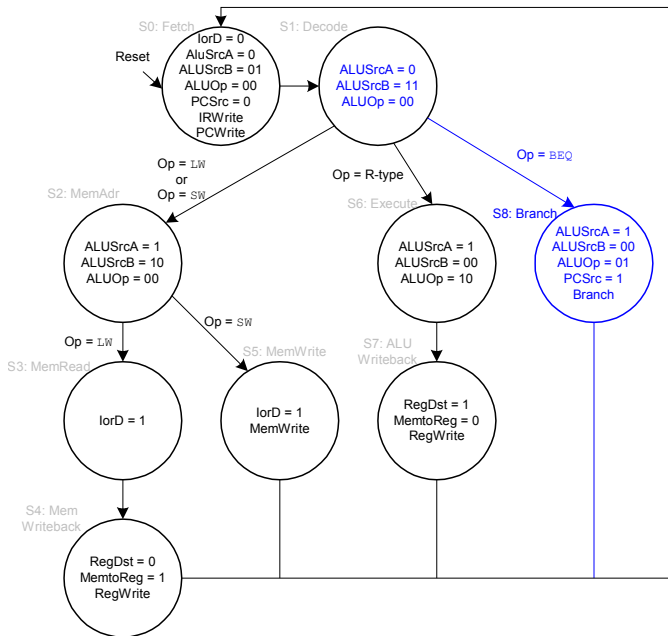


# Controller Behavior

 

 
# Controller Behavior

Additional circuitry for the jump instruction




# Controller Behavior

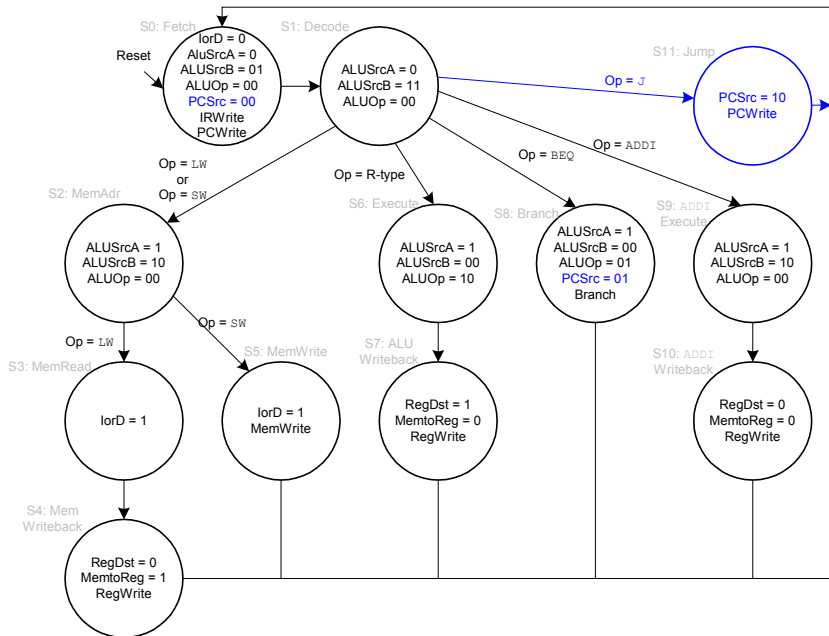




# Multicycle Critical Path

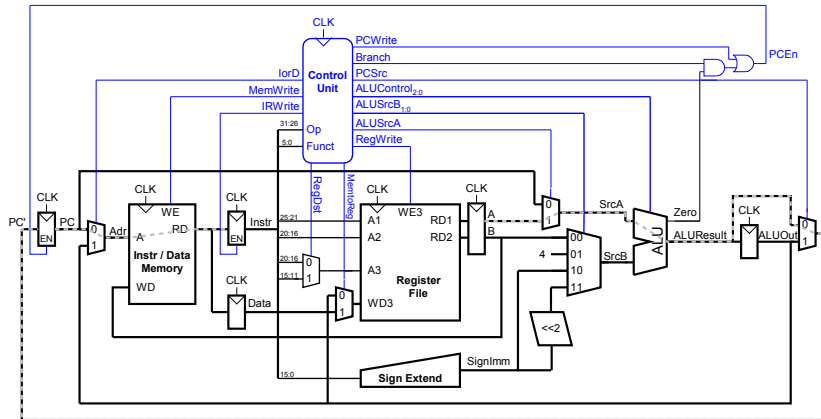

Two hypotheses: Reading memory or going through the ALU

# Multicycle Clock Period

Element	Delay
Register clk-to-Q	$t_{pcq-PC}$ 30 ps
Register setup	$t_{setup}$ 20
Multiplexer	$t_{mux}$ 25
ALU	$t_{ALU}$ 200
Memory Read	$t_{mem}$ 250
Register file read	$t_{Rfread}$ 150
Register file setup	$t_{RFsetup}$ 20

 

$$\begin{aligned}
 T_C &= t_{pcq-PC} + t_{mux} + \max\{t_{ALU} + t_{mux}, t_{mem}\} + t_{RFsetup} \\
 &= (30 + 25 + \max\{200 + 25, 250\} + 20) \text{ ps} \\
 &= 325 \text{ ps} \\
 &= 3.08 \text{ GHz}
 \end{aligned}$$

vs. 925 ps for our single-cycle processor

# Execution Time for Our Multi-Cycle Processor

For a 100 billion-instruction task on our multi-cycle processor, each instruction takes 4.12 cycles on average. With a 325 ps clock period,

$$\begin{aligned}\frac{\text{Seconds}}{\text{Program}} &= \frac{\text{Instructions}}{\text{Program}} \times \frac{\text{Clock Cycles}}{\text{Instruction}} \times \frac{\text{Seconds}}{\text{Clock Cycle}} \\ &= 100 \times 10^9 \times 4.12 \times 325 \text{ ps} \\ &= 133.9 \text{ seconds}\end{aligned}$$

vs. 92.5 seconds for our single-cycle processor.