
 


Fundamentals of Computer Systems

Sequential Logic



Harris and Harris
Chapter 3.1-3.3,3.5

Bistable Elements

 


Equivalent circuits; right is more traditional.

Two stable states:

  


RS Latch

 

R	S	Q	\bar{Q}
0	0		
0	1		
1	0		
1	1		


RS Latch

 

R	S	Q	\bar{Q}
0	0		
0	1	1	0
1	0		
1	1		


Set ($Q = 1$)

RS Latch

 


R	S	Q	\bar{Q}	
0	0			
0	1	1	0	Set ($Q = 1$)
1	0	0	1	Reset ($Q = 0$)
1	1			

RS Latch

 


R	S	Q	\bar{Q}	
0	0	Q	\bar{Q}	Hold previous value
0	1	1	0	Set ($Q = 1$)
1	0	0	1	Reset ($Q = 0$)
1	1			

RS Latch

 


R	S	Q	\bar{Q}	
0	0	Q	\bar{Q}	Hold previous value
0	1	1	0	Set ($Q = 1$)
1	0	0	1	Reset ($Q = 0$)
1	1	0	0	Bad. Do not use.

$\overline{R}\overline{S}$ Latch

 

\overline{R}	\overline{S}	Q	\overline{Q}	
0	0	1	1	Bad. Do not use.
0	1	0	1	Reset ($Q = 0$)
1	0	1	0	Set ($Q = 1$)
1	1	Q	\overline{Q}	Hold previous value


D Latch

 

C	D	Q	\overline{Q}
0	X	Q	\overline{Q}
1	0	0	1
1	1	1	0

A Challenge: Build a traffic light controller

 Want the lights to cycle green-yellow-red.




Does this work?











 








 

 


 

 


 


Positive-Edge-Triggered D Flip-Flop

 


C	_____
D	████████
C_M	<u>transparent</u>
D'	████████
C_S	<u>opaque</u>
Q	_____


Positive-Edge-Triggered D Flip-Flop

  


Positive-Edge-Triggered D Flip-Flop

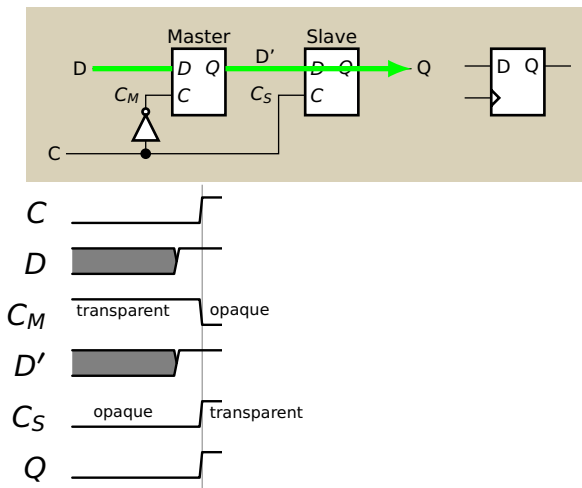


Positive-Edge-Triggered D Flip-Flop

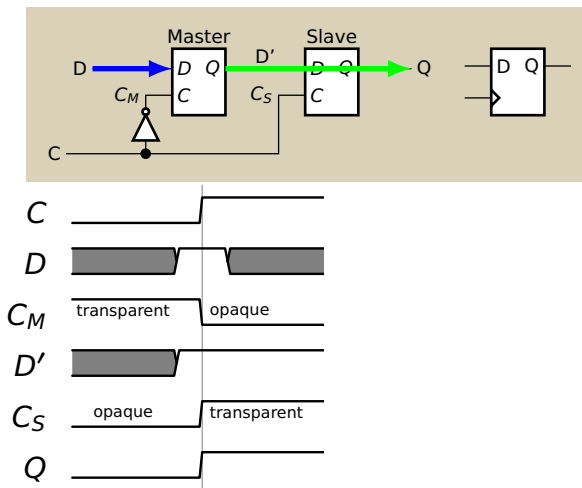

Positive-Edge-Triggered D Flip-Flop

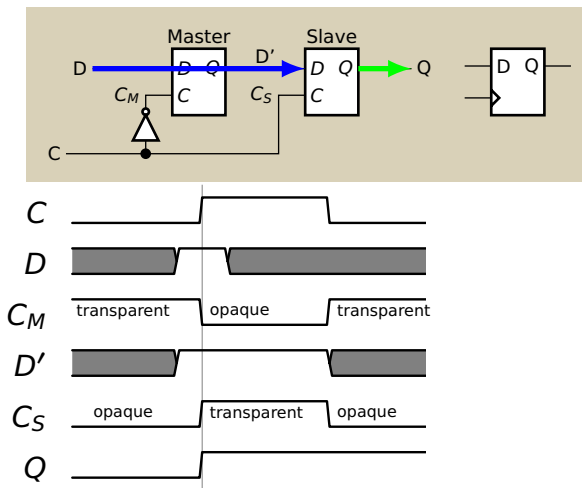


Positive-Edge-Triggered D Flip-Flop

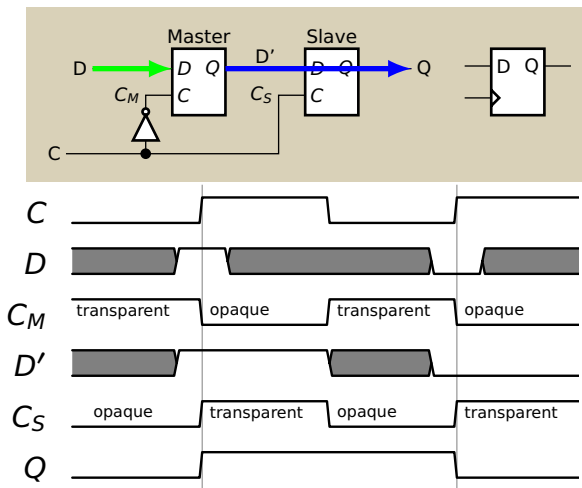

The Traffic Light Controller: A second try

Let's try this again with D flip-flops.

 

CLK__



R__

Y__

G__



The Traffic Light Controller: A second try

Let's try this again with D flip-flops.

  



The Traffic Light Controller: A second try

Let's try this again with D flip-flops.

  



The Traffic Light Controller: A second try

Let's try this again with D flip-flops.

  


The Traffic Light Controller: A second try

Let's try this again with D flip-flops.

 
 


The Traffic Light Controller with Reset


 


CLK _____
RESET _____
R ☐
Y ☐
G ☐



The Traffic Light Controller with Reset

  



The Traffic Light Controller with Reset

  



The Traffic Light Controller with Reset

  


The Traffic Light Controller with Reset

  


The Traffic Light Controller with Reset

  

D Flip-Flop with Enable


 


<i>C</i>	<i>E</i>	<i>D</i>	<i>Q</i>
↑	0	X	<i>Q</i>
↑	1	0	0
↑	1	1	1
0	X	X	<i>Q</i>
1	X	X	<i>Q</i>

 


What's wrong with this solution?

Asynchronous Preset/Clear

  

 The Traffic Light Controller w/ Async. Reset




The Synchronous Digital Logic Paradigm


Gates and D
flip-flops only

Each flip-flop
driven by the
same clock

 Every cyclic
path contains
at least one
flip-flop




 Cool Sequential Circuits: Shift Registers



A	Q_0	Q_1	Q_2	Q_3
0	X	X	X	X
1	0	X	X	X
1	1	0	X	X
0	1	1	0	X
1	0	1	1	0
0	1	0	1	1
0	0	1	0	1
0	0	0	1	0
1	0	0	0	1
0	1	0	0	0

Universal Shift Register

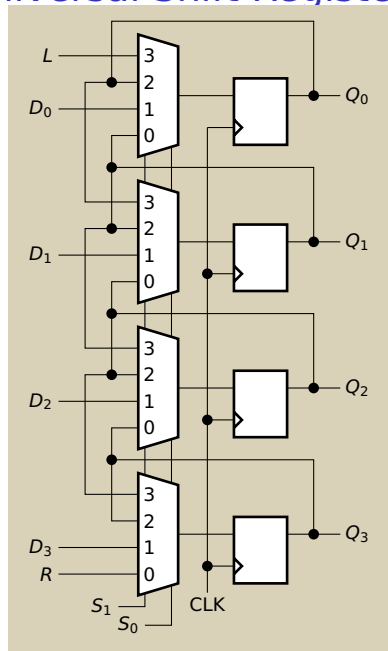


S_1	S_0	Q_3	Q_2	Q_1	Q_0
0	0	R	Q_3	Q_2	Q_1
0	1	D_3	D_2	D_1	D_0
1	0	Q_3	Q_2	Q_1	Q_0
1	1	Q_2	Q_1	Q_0	L

S_1	S_0	Operation
0	0	Shift right
0	1	Load
1	0	Hold
1	1	Shift left


Cool Sequential Circuits: Counters

 Cycle through sequences of numbers, e.g.,



Flip-Flop Timing

 
Setup Time: Time before the clock edge after which the data may not change



Flip-Flop Timing

Setup Time: Time before the clock edge after which the data may not change

 
Hold Time: Time after the clock edge after which the data may change



Flip-Flop Timing

Setup Time: Time before the clock edge after which the data may not change

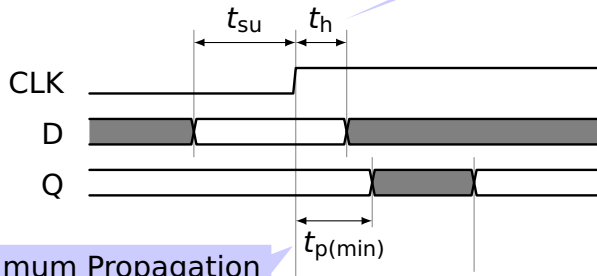Hold Time: Time after the clock edge after which the data may change




Minimum Propagation Delay: Time from clock edge to when Q might start changing

Flip-Flop Timing

Setup Time: Time before the clock edge after which the data may not change


 
Hold Time: Time after the clock edge after which the data may change



Minimum Propagation Delay: Time from clock edge to when Q might start changing


Maximum Propagation Delay: Time from clock edge to when Q guaranteed stable

Timing in Synchronous Circuits

  


t_c : Clock period. E.g., 10 ns for a 100 MHz clock

Timing in Synchronous Circuits


 


Sufficient Hold Time?

 


Hold time constraint: how soon after the clock edge is
D liable to start changing?
Min. FF delay + min. logic delay

Timing in Synchronous Circuits

  


Setup time constraint: when before the clock edge is D guaranteed to have stabilized?
Max. FF delay + max. logic delay

Clock Skew: What Really Happens

 


Sufficient Hold Time?

 


CLK_2 arrives late, creating potential hold time violation

Clock Skew: What Really Happens

 

Sufficient Setup Time?

 

CLK_2 arrives early, creating potential setup time violation